

Note: There are 3 Questions (Question1: 0.75Mark, Question2: 0.5Mark, Question3: 0.75Mark)

Question I:

(a) A circuit consists of two resistors with resistances $R_1 = 6.0 \Omega$ and $R_2 = 1.5 \Omega$, a variable resistor, the resistance R_{var} of which can be adjusted, a resistor of unknown value R_u , and 9.0 volt battery connected as shown in the figure. When R_{var} is adjusted to 12 ohms, there is zero current through the ammeter.

1. What is the unknown resistance R_u ?

2. Calculate the value of ΔR_u

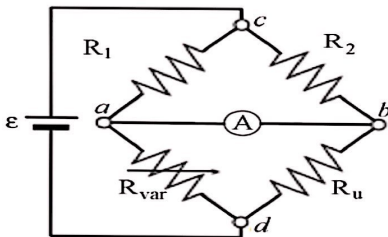



Figure1: Wheatstone bridge circuit

(b) If $R_1 = 1 \Omega$, $R_2 = 2 \Omega$, and $R_u = 3 \Omega$, to what value should R_{var} be adjusted so as to achieve a balanced condition?

Question II:

For the Wheatstone bridge circuit of the following Figure , solve the following problem:

If $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 1.5\Omega$, $V_0 = 6\text{ V}$, $R_a = 0.1\Omega$, and R_x were then to deviate by a small amount to $R_x = 3.01\Omega$, what would be the reading on the ammeter?

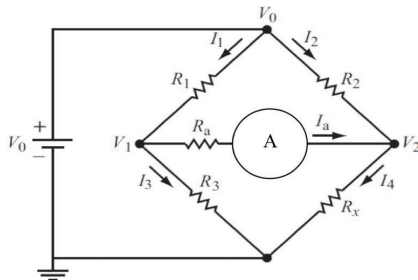

Question III:

a) The AC Bridge of the following figure (Figure2) nulls with $R_1=1k\Omega$, $R_2=2k\Omega$, $R_3=100\Omega$ and $L_3=250mH$.

1. Find the values of R_4 and L_4 .

2. Calculate the value of ΔR_4 and ΔL_4

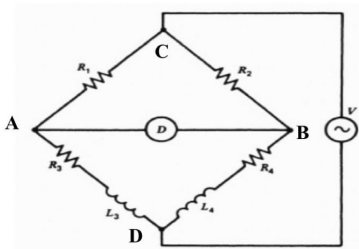


Figure2: AC Bridge

b) Consider The AC Bridge of the Figure2 but replace

- The branch BD by capacitance C_4 connected in series with R_4 .
- And L_3 by $C_3=10\mu F$.

Find the values of R_4 and C_4 .